



CIRCUITS: INTRODUCTION

- Some electronics
- From Boolean algebra to circuits



Voltage has to be considered with a lot of attention because power P verifies:

$$P = \alpha C V^2 f$$

C : circuit capacitance

V : Supply voltage

f : Frequency;

Furthermore $f = \gamma V$.

Therefore Power varies as a cubic function of Voltage.

High voltage has three corollaries:

- High power therefore hot chips requiring specific cooling system
- High energy consumption therefore shorter battery life
- High frequencies (overclocking 😊)




MOS = Metal Oxide Semiconductor

two types: n-type and p-type

n-type

when Gate has positive voltage (Logical 1),
short circuit between #1 and #2
(switch closed)

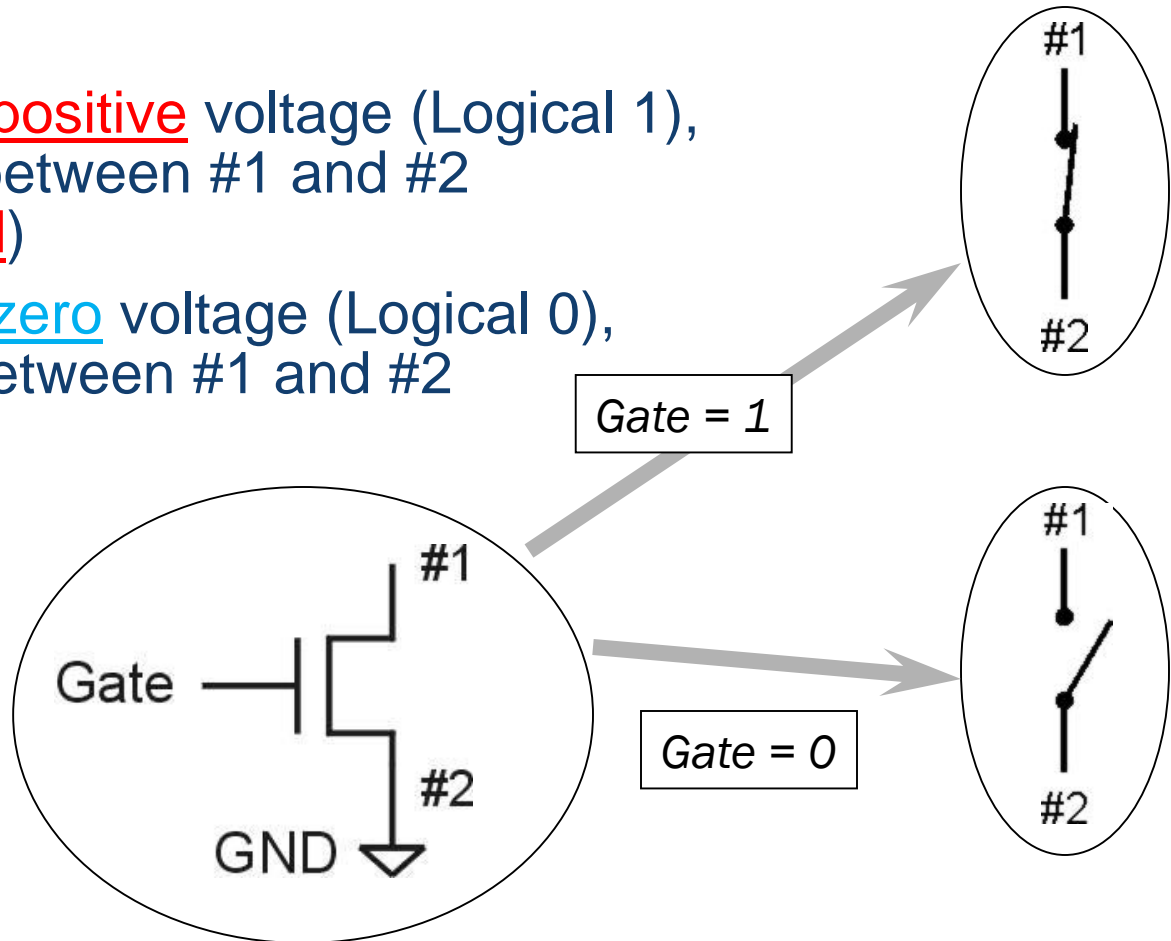when Gate has zero voltage (Logical 0),
open circuit between #1 and #2
(switch open)










p-type is *complementary* to n-type

when Gate has **positive** voltage (Logical 1)
open circuit between #1 and #2
(switch **open**)

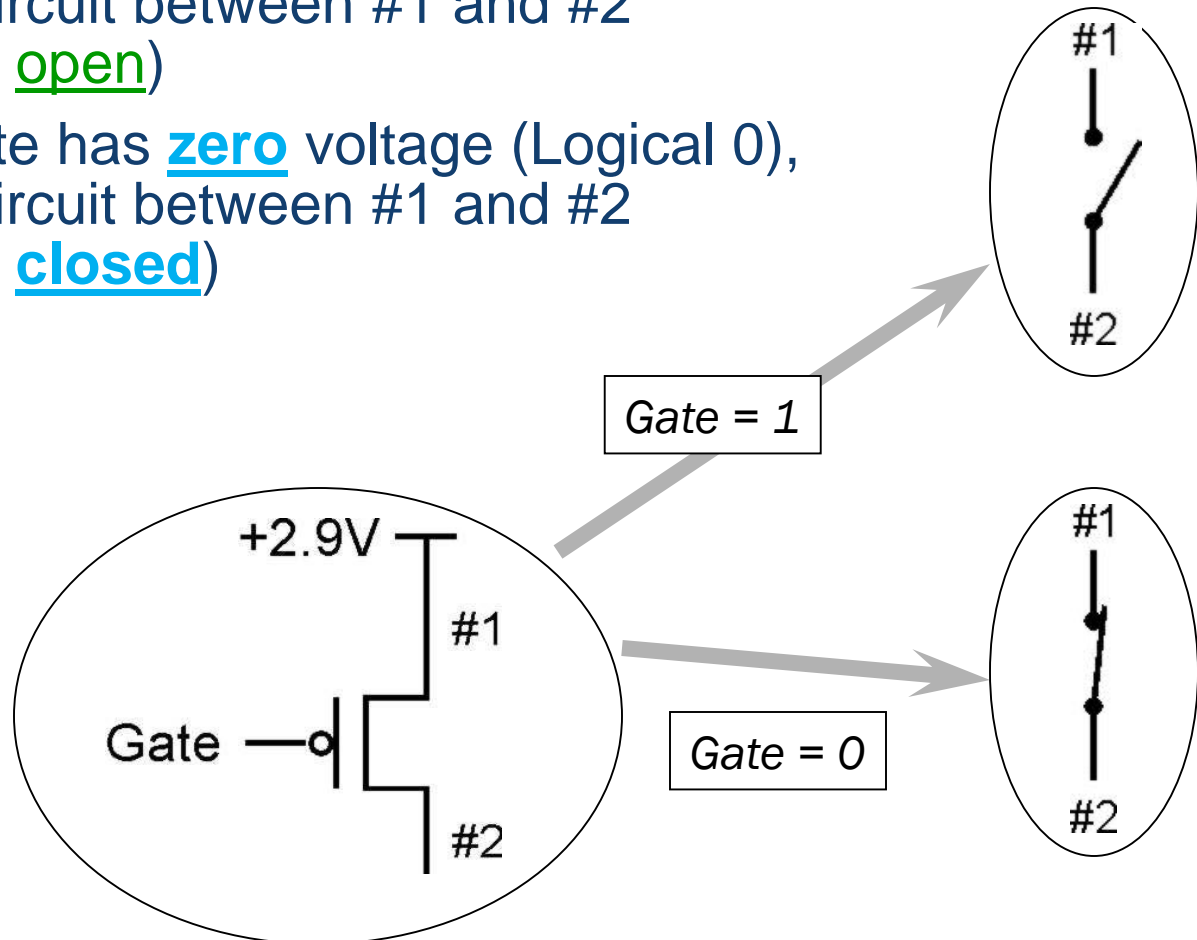when Gate has **zero** voltage (Logical 0),
short circuit between #1 and #2
(switch **closed**)




   

 

WARNING: the symbols used for the N Type and P Type transistors is different!!


CMOS NOR GATE BEHAVIOR

 


A	B	C = NOR(A,B)
0	0	1
0	1	0
1	0	0
1	1	0

SOURCE OF THE DRAWINGS: <http://www.quadibloc.com/comp/cp01.htm>


INTEGRATED CIRCUIT LAYOUT OF A NOR GATE

 

 - n⁺-type
- p⁺-type
- polysilicon
- metal
- interconnect
- n-type
- p-type




 SOURCE OF THE DRAWINGS: <http://www.quadibloc.com/comp/cp01.htm>




A	F
L	H
H	L

CMOS INVERTER

 


A	B	F
L	L	H
L	H	H
H	L	H
H	H	L

CMOS NAND

 


A	B	F
L	L	H
L	H	L
H	L	L
H	H	L

CMOS NOR

 

A	B	F
L	L	L
L	H	L
H	L	L
H	H	H

CMOS AND

 


A	B	F
L	L	L
L	H	H
H	L	H
H	H	H

CMOS OR

SOURCE OF THE DRAWINGS: <https://learn.digilentinc.com/Documents/313>


THE PHYSICAL LAYOUT OF A CMOS NAND

 


SOURCE OF THE DRAWINGS : WIKIPEDIA




AND/OR/NOT STANDARD REPRESENTATION

 


ANSI/MIL AND

 


ANSI/MIL OR

 


ANSI/MIL NOT

 

IEC AND

 


IEC OR

 


IEC NOT




NAND/NOR/XOR/XNOR REPRESENTATIONS

 


MIL/ANSI NAND

 


MIL/ANSI NOR

 


ANSI/MIL XOR

 


ANSI/MIL XNOR

 


IEC NAND

 

IEC NOR

 


IEC XOR

 

IEC XNOR





EUROPEAN, US AND GERMAN NORMS

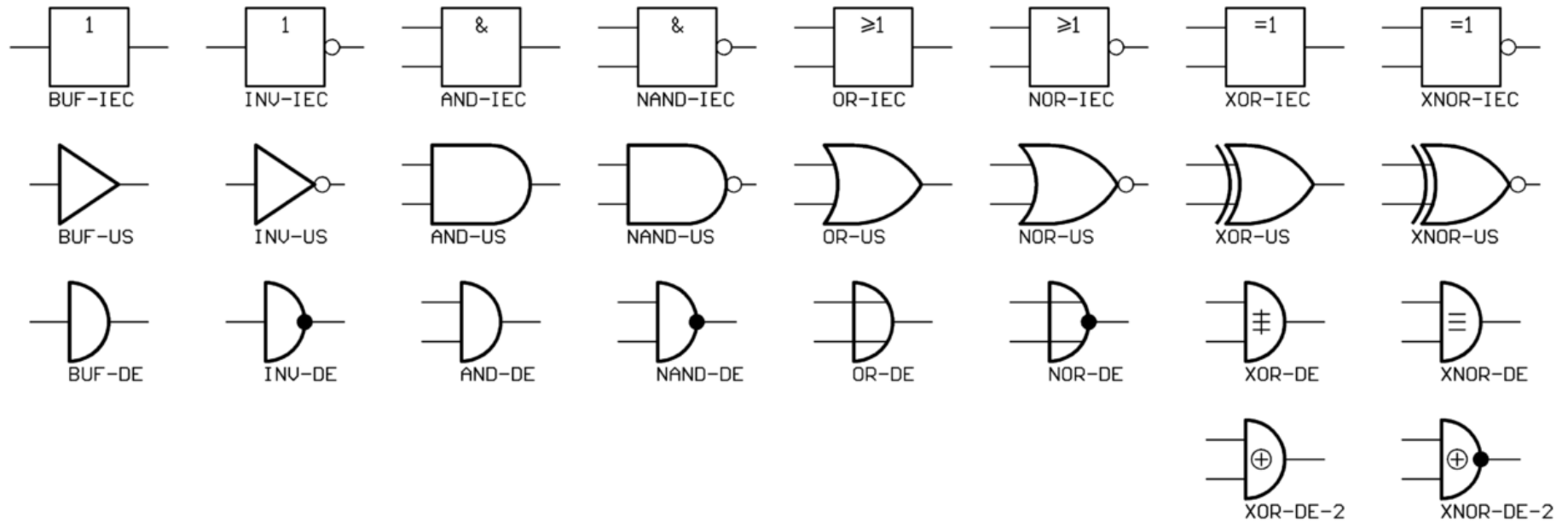

A PROPOSAL FOR EASY GATE DRAWING




  Simply use rectangles and write inside the corresponding boolean function!! Non ambiguous and easy to draw.






AND IMPLEMENTATIONS USING NAND / NOR

 

AND Using NAND gates

$$((ab)'(ab)')' = ((ab)')' = ab$$

 


AND Using NOR gates


$$((a+a)' + (b+b)')' = (a' + b')' = ab$$



 NAND (resp. NOR) USING NOR (resp. NAND) GATES



 NAND IMPLEMENTED USING NOR GATES
1 NAND NEEDS 4 NOR GATES



NOR IMPLEMENTED USING NAND GATES:
1 NOR NEEDS 4 NAND GATES




Given a truth table

1. Write the Boolean expression
2. Make the Boolean expression simpler (minimal SOP)
3. Draw as gates

Example:

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1
 
$$\begin{aligned}
 F &= a'bc' + a'bc + ab'c + abc \\
 &= a'b(c' + c) + ac(b' + b) \\
 &= a'b + ac
 \end{aligned}$$






AND/OR can take any number of inputs.

AND = 1 if all inputs are 1, 0 otherwise: $\text{AND}(a,b,c) = abc$

OR = 1 if any input is 1, 0 otherwise $\text{OR}(a,b,c) = a+b+c$


This can be extended to NAND/NOR. This is directly derived from operators associativity

 Can implement with multiple two-input gates, or with single CMOS circuit.





VARIOUS IMPLEMENTATIONS OF MULTI-INPUT

 



de Morgan's

Standard form:

$$a'b' = (a + b)'$$

$$a' + b' = (ab)'$$

Inverted:

$$a + b = (a'b')'$$

$$(ab)' = (a' + b')$$



AND with complemented inputs \equiv NOR

OR with complemented inputs \equiv NAND

OR \equiv NAND with complemented inputs

AND \equiv NOR with complemented inputs

**pushing
the
bubble**

 
 




Example: AND/OR network to NOR/NOR

$$\begin{aligned}
 Z &= ab + cd \\
 &= (a' + b')' + (c' + d')' \\
 &= \{[(a' + b')' + (c' + d')']\}' \\
 &= \{[((a')' \cdot (b')') + ((c')' \cdot (d')')]\}'
 \end{aligned}$$

≡ NOR

  





TRANSFORMING SOP'S INTO A BUNCH OF NANDS



AND/OR to NAND/NAND

  On all wires, at both ends, add an inverter. At the input of the NAND gates, replace NOT by NAND





A lot of material was found in Wikipedia.

Some of these slides were inspired by slides developed by:

- University of Washington Computer Science & Engineering (CSE 370)
- Y.N. Patt (Univ of Texas Austin)
- S. J. Patel (Univ of Illinois Urbana Champaign)
- Walid A. Najjar (Univ California Riverside)
- Brian Linard (Univ California Riverside)
- G.T. Byrd (Univ North Carolina)